

UNIT 2 : IO PORT INTERFACING - I

Syllabus :

Pin Diagram and its functioning, Port structure,

IO Interfacing Requirements

Interfacing of : LED

keys

Seven segment Multiplexed Display

DAC 0808

ADC 0809

Stepper Motor

Relay

Buzzer

Opto Isolator

Design of Data Acquisition System (DAS) :

All programs in C Language.

Text Book :

Mahumad Ali Mazidi, Janice Gillispie Mazidi, Rolin D McKin

"The 8051 microcontroller & Embedded systems", PHI 2nd Edition

L IO Interfacing

All 8051 Microcontrollers have 4 I/O ports each comprising of 8 bits, which can be configured as inputs or outputs.

32 I/O pins available, enabling the microcontroller to be connected to peripheral devices.

Pin configuration i.e whether the port is to be configured as an input (1) or an output (0) depends on its logic state.

In order to configure a microcontroller pin as input it is necessary to apply a logic 1 to appropriate I/O port bit.

Similarly in order to configure a microcontroller pin as output it is necessary to apply a logic 0 to appropriate I/O port bit.

L Port Structure:

Port 0:

Address : 80H

Port 0 is used as simple I/O port.

Pull Register is needed when Port 0 is defined as output port because Port 0 is open drain.


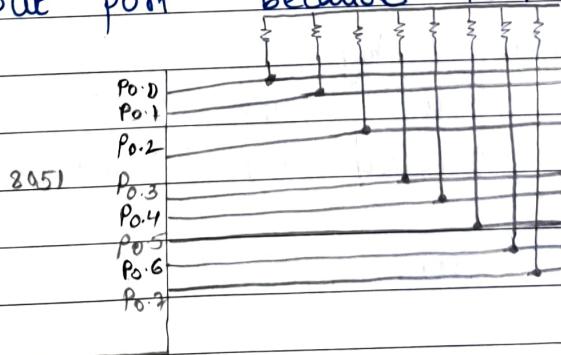


fig: Port0 with Pull up Register.

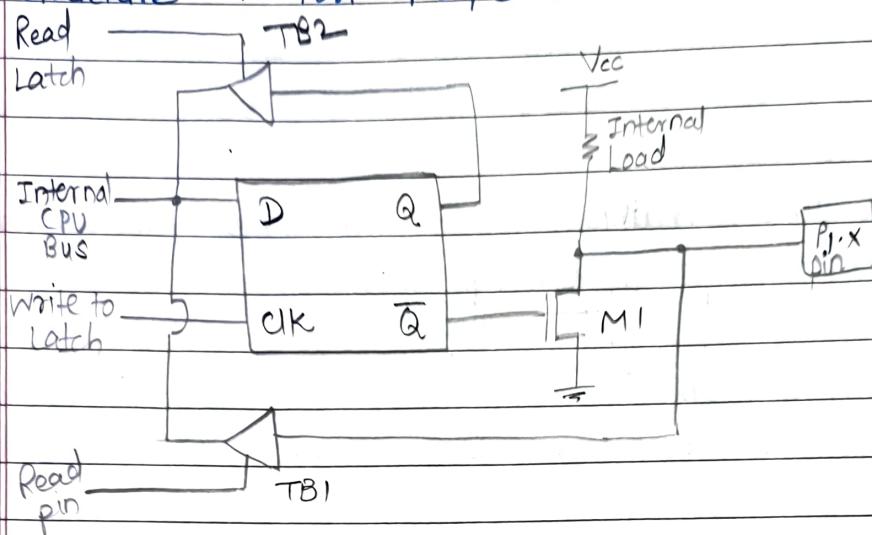Structure of Port 1, 2, 3 of 8051 Microcontroller.



Each I/O port is Connected internally to CPU bus.

The bit latch (one bit in port's SFR) is represented as D flip-flop, which clocks a input from the internal bus in response to "write to latch" signal from CPU

The Q output of flip flop is placed on internal bus in response to "read latch" signal from CPU.

The level of port pin itself is placed on the internal bus in response to "read pin" signal from CPU.

Tri state Buffer

TB1 is controlled by "Read Pin"

Read Pin = 1 → Read Data at Pin

TB2 is controlled by "Read Latch"

Read Latch = 1


Read Value from internal latch.

A transistor M1

Gate = 0 open

Gate = 1 close

Reading "low" at i/p pin:

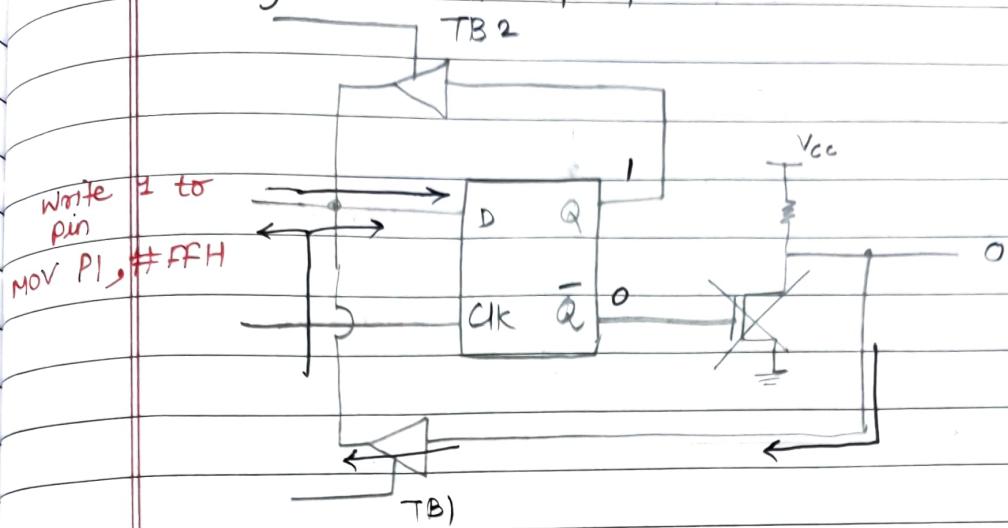


Read Pin = 1

Read Latch = 0

Write to Latch = 1

Reading "High" at input pin:

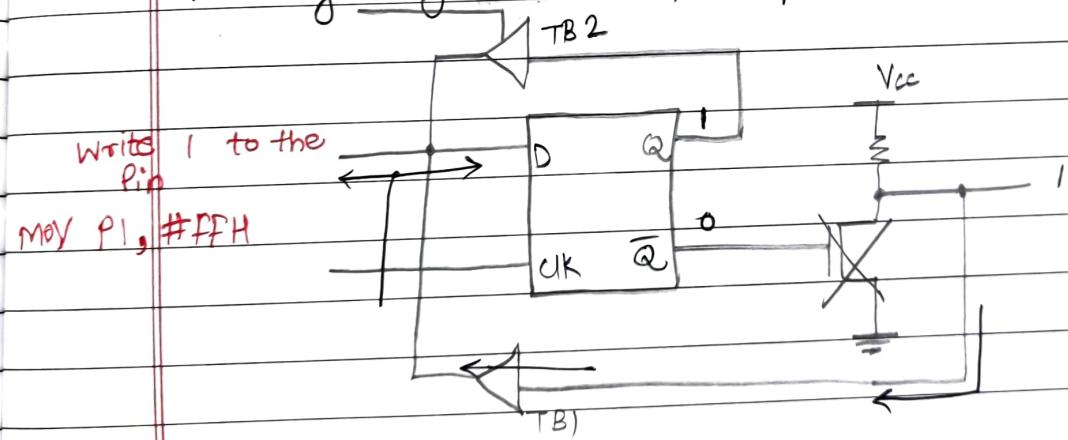


Read Pin = 1

Read Latch = 0

Write to Latch = 1


Writing '0' to o/p pin PI-X

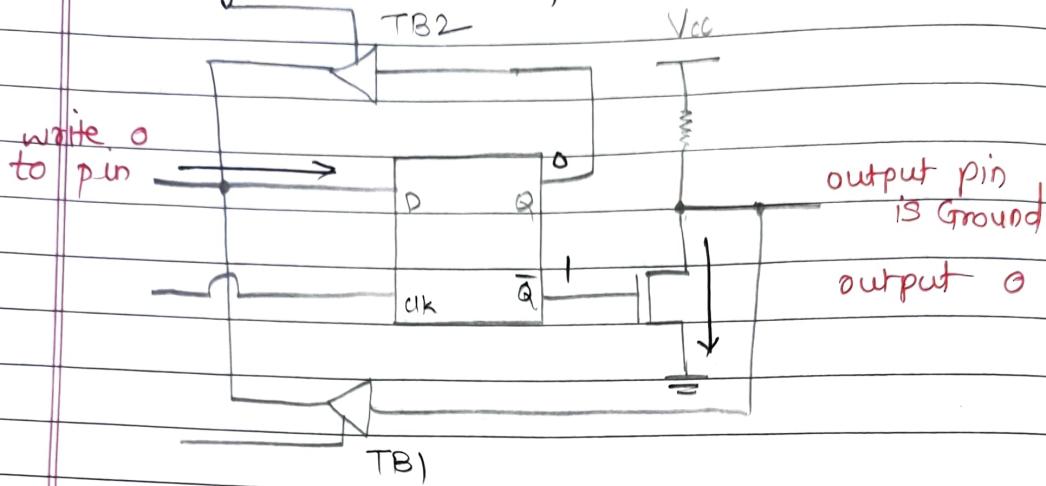

Writing 0 to o/p pin PI-X

Read Latch

Internal

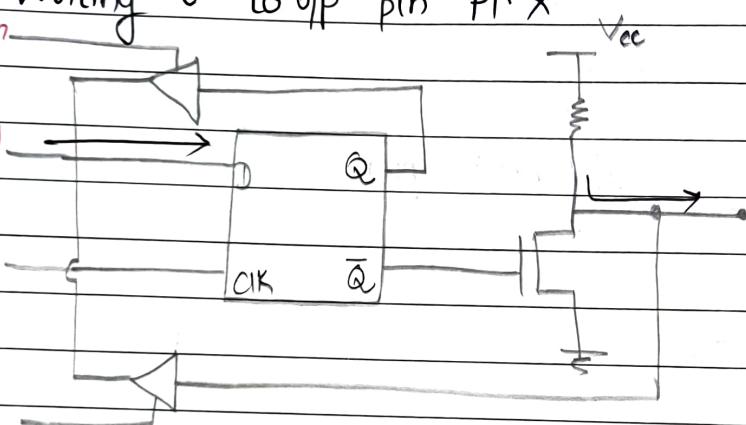

L LED's

LED is semiconductor device.

LED's Convert Electrical energy into light energy.

symbol :



why LED's ?

low power Consumption


Small size

fast switching


physically Robust

Long Lasting

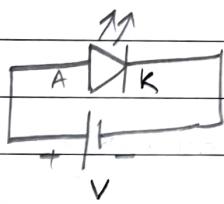LED's are available in different colors like Red, Blue, Green, Yellow, white etc.




LED ON

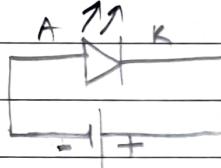

LED off

Single LED interfacing :

Method 1 :

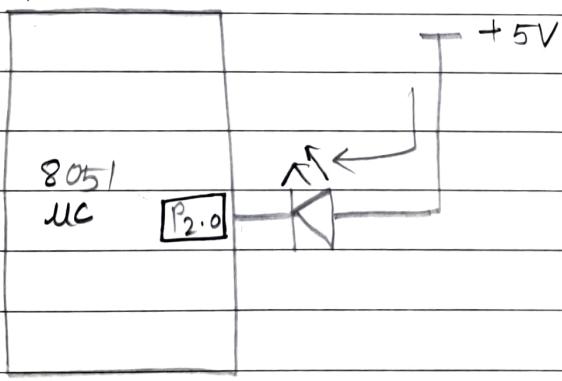

Common Anode

To make LED = ON
P_{2.0} should be given 0

To make LED = OFF

P_{2.0} should be given 1

LED flashing on P2.0

```
#include <reg51.h>
```

```
sbit LED = P2^0 ;
```

```
void delay()
```

{

```
unsigned int i, j ;
```

```
for (i = 0 ; i < 1000 ; i++)
```

{

```
for (j = 0 ; j < 10,000 ; j++)
```

{

{

}

```
void main()
```

{

```
while (1)
```

// Do it continuously

```
    LED = 0 ;
```

// LED ON

```
    delay();
```

```
    LED = 1 ;
```

// LED OFF.


```
    delay();
```

}

{

Single LED interfacing with 8051

Method 2 :

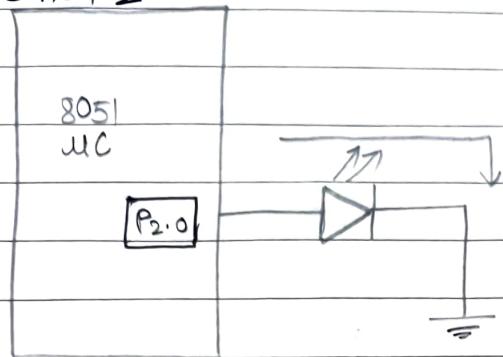

Common Cathode

LED flashing on P2.0

```
#include <reg51.h>
sbit LED = P2^0;
```

Void delay()

{

 Unsigned int i, j;

 for (i=0 ; i<1000 ; i++)

{

 for (j=0 ; j<10,000 , j++)

{

}

}

Void main()

{

 while (1)

{

 LED = 1; // LED ON

 delay();

 LED = 0; // LED OFF


 delay();

}

Multiple LED interfacing with 8051

LED's in Common Cathode connected to Port 2

Interfacing Diagram :

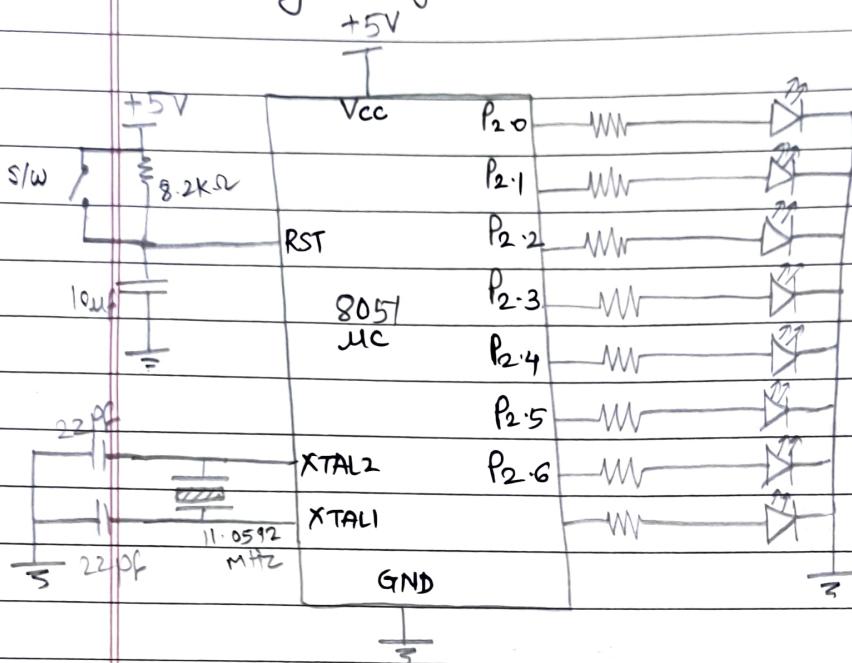

LED flashing on P2

```
#include <reg51.h>
```

```
Void delay()
```

```
{
```

```
unsigned int i,j;
```

```
for (i=0; i<300; i++)
```

```
{
```

```
for (j=0; j<=1000; j++)
```

```
{
```

```
{
```

```
{
```

```
Void main()
```

```
{
```

```
while (1)
{
```

```
P2 = 0xFF; // LED ON
```

(common cathode)

```
delay();
```

```
P2 = 0x00;
```

```
delay();
```

// LED OFF.

```
}
```

Multiple LED interfacing with 8051 (Alternate blinking)

Referr same interfacing Diagram:

Logic for Alternate LED Blinking on P2

$\begin{array}{cccccc} 0 & & 0 & & 1 & \\ \underbrace{\hspace{1cm}}_5 & \underbrace{\hspace{1cm}}_5 & & & & \end{array}$	$= 55H$
--	---------

$\begin{array}{cccccc} 1 & & 0 & & 0 & \\ \underbrace{\hspace{1cm}}_A & \underbrace{\hspace{1cm}}_A & & & & \end{array}$	$= AA H$
--	----------

```
#include <reg51.h>
```

```
Void delay()
```

```
{
```

```
unsigned int i,j;
```

```
for (i=0 ; i<300 ; i++)
```

```
{
```

```
for (j=0 ; j<1000 ; j++)
```

```
{
```

```
}
```

```
}
```

Void main ()

{

while (1)

{

P2 = 0X55 ;

delay ();

P2 = 0XAA;

delay ();

{


}

↳ Seven Segment Display :

Seven Segment Display uses Seven LEDs to make any Digit.

If all LEDs are ON it shows Digit 8.

There are Two types of SSD :

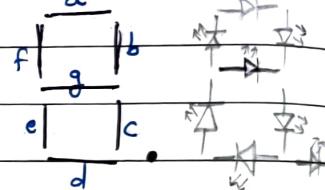

Common Cathode :

Cathode of all LEDs is given as a Common pin.

The Anode is Connected to port pins


Common Cathode method requires port pins to source

Large current . But 8051 cannot Source current beyond 2mA.

Common Anode :

Anode of all LEDs are given as common pin . In this case Cathode is connected to port pins . Hence port pin have to sink 20 mA current.

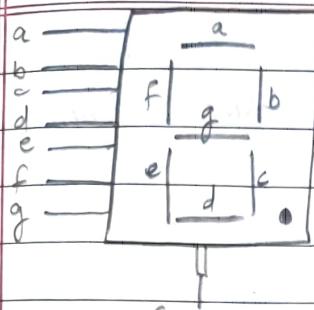
Hence we can use Common anode Seven Segment Display and Connect to 8051.



Common Cathode

0 → OFF LED

1 → ON LED

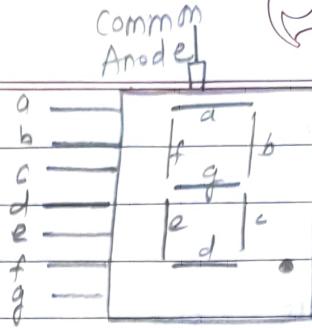
fig: Common Cathode
LED SSD

0 → GLOW LED

1 → OFF LED

fig: Common Anode
LED SSD

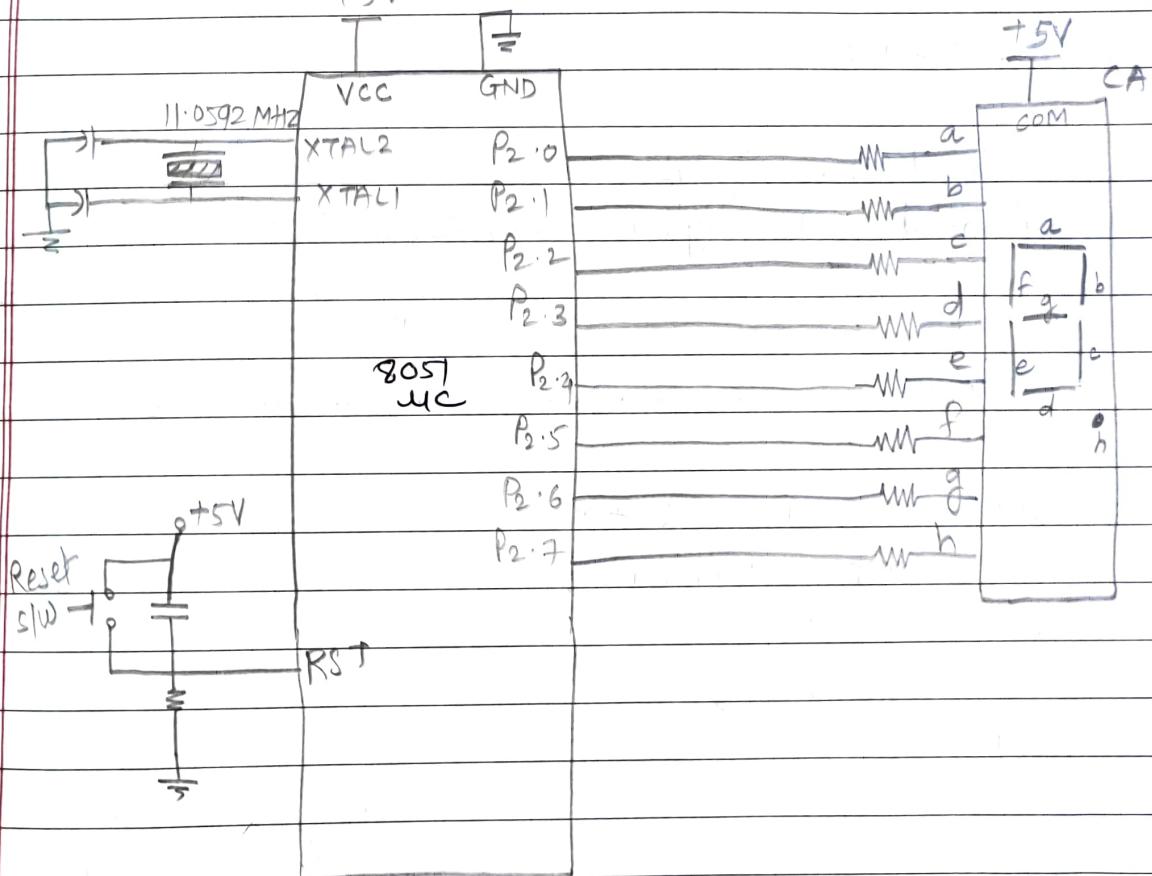7 segment Display Interfacing Diagram (common Anode)



Program to Display 0 to 9 Digits Continuously on Seven Segment Display (Decade Counter) Connected to P2

```
#include <reg51.h>
```

```
Void delay()
```

```
{
```

```
int j;
```

```
for (j=0 ; j<=1000 ; j++)
```

```
{
```

```
}
```

```
}
```

```
Void main()
```

```
{
```

```
Unsigned char i, dat;
```

```
Unsigned int digit [] = {0xCO, 0xF9, 0XA1, 0XB0, 0X99,
```

```
0X92, 0X82, 0XF8, 0X80, 0X90}
```

```
while (1)
```

```
{
```

```
for (i=0 ; i<10 ; i++)
```

```
{
```

```
dat = digit [i];
```


```
P2 = dat;
```

```
delay();
```

```
}
```

```
}
```

```
}
```

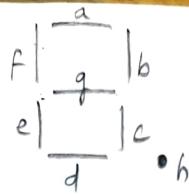

Common Anode
0 → ON
1 → OFF


classmate

Date _____

Page _____

Digit	b	g	f	e	d	c	b	a	Hex Value
0	1	1	0	0	0	0	0	0	C0
1	1	1	1	1	1	0	0	1	fg
2	1	0	1	0	0	1	0	0	A4
3	1	0	1	1	0	0	0	0	B0
4	1	0	0	1	1	0	0	1	99
5	1	0	0	1	0	0	1	0	g2
6	1	0	0	0	0	0	1	0	82
7	1	1	1	1	1	0	0	0	F8
8	1	0	0	0	0	0	0	0	80
9	1	0	0	1	0	0	0	0	90

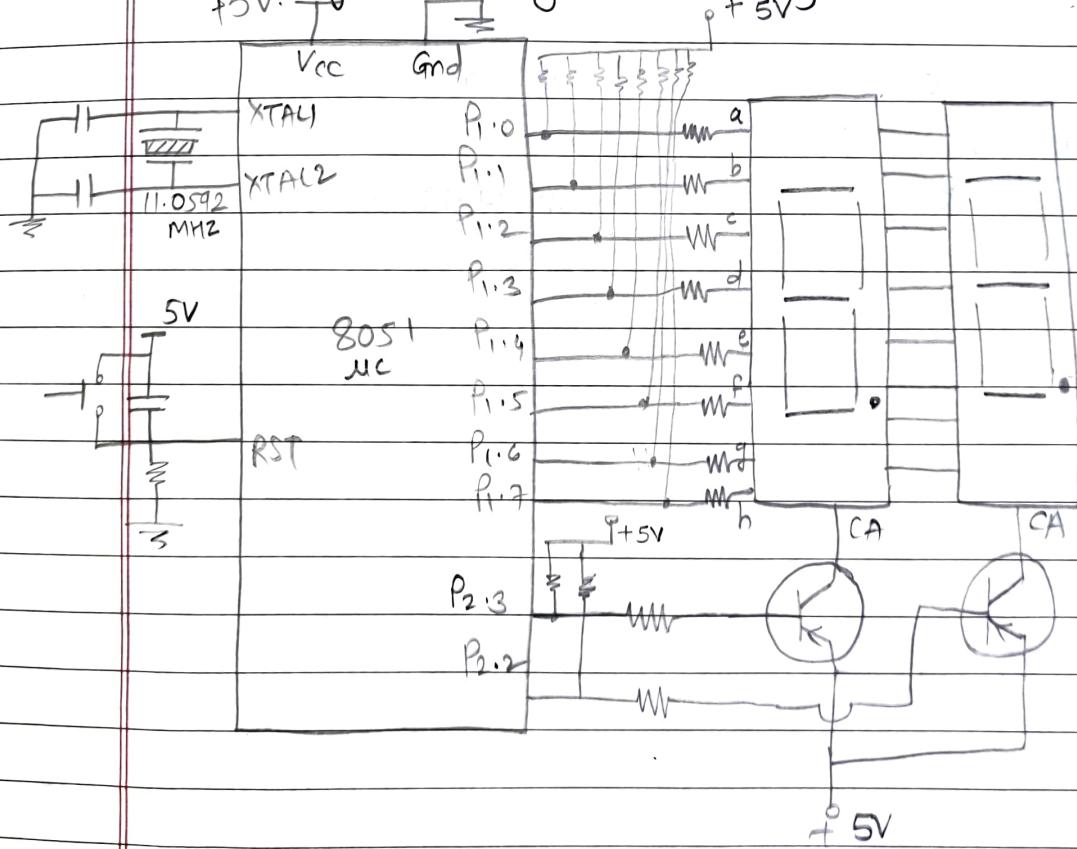Multiplexing 7 segment Display to 8051 to display "99"



Display gg on seven segment display

```
#include <reg51.h>
```

```
Void delay ()  
{
```


```
    int i ;  
    for ( i=0 ; i<1000 ; i++ )  
    {  
    }  
}
```

```
Void main ()  
{
```

```
    while (1)  
{
```

```
        P1 = 0x90 ; // value of g  
        delay ()
```

```
}
```

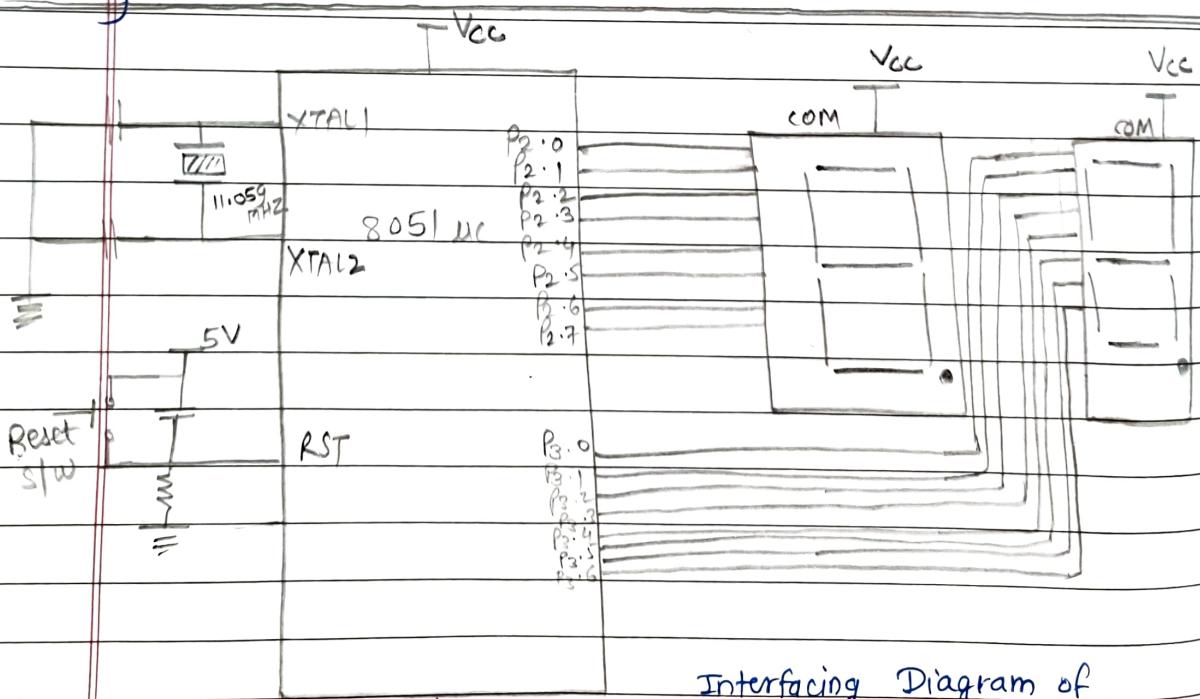

Interfacing Diagram of
fig: Multiplexed Seven Segment Display to
count 0 to gg

Count from 0 to 99 using 8051 mc with seven segment display

```
#include <reg51.h>
Void delay();
Void main()
{
    Unsigned int ch[] = {0x00, 0xF9, 0xA4, 0xB0, 0x99,
                         0x92, 0x82, 0xF8, 0x80, 0x90};
    Unsigned int i, j;
    P3 = 0x00;
    P2 = 0x00;

    while(1)
    {
        for (j = 0; j < 10; j++)
        {
            for (i = 0; i < 10; i++)
            {
                P3 = ch[i];
                delay();
                if (j != 10)
                    P2 = ch[j + 1];
                if (i == 10 && j == 10)
                    P2 = 0x00;
                P2 = 0x00;
            }
        }
    }
}

Void delay()
{
    int i;
    for (i = 0; i < 1000; i++)
}
```

ADC 0808/0809.

ADC 0808/0809 with 8 analog channels:

JN3 → 1		28 ← JN2
JN4 → 2		27 ← JN1
JN5 → 3		26 ← JN0
JN6 → 4		25 ← A
JN7 → 5	ADC	24 ← B
START → 6	0808	23 ← C
EOC ← 7	0809	22 ← ALE
D3 ↔ 8		21 → D7
OE → 9		20 → D6
CLOCK → 10		19 → D5
Vcc → 11		18 → D4
Vref(+) → 12		17 → D0
Gnd ← 13		16 → Vref (-)
D1 ← 14		15 → D2

Fig : Pin diagram of ADC IC 0808/0809

It has 8 analog channels (JN0 - JN7)

User can connect Analog signal input to this 8 channels and IC will convert Analog to Digital signal.

This channels are internally multiplexed. At a time IC will select one input channel and convert to Digital.

To select channel, IC has address lines (A, B, C)
Each channel has Unique address.

Analog Channel Address.

Channel	C	B	A
IN0	0	0	0
IN1	0	0	1
IN2	0	1	0
IN3	0	1	1
IN4	1	0	0
IN5	1	0	1
IN6	1	1	0
IN7	1	1	1

After placing address of particular channel on address bus user has to latch this address. So for that ALE signal is used. User has to give low to high pulse to ALE to latch the address.

Now User can send the start of conversion signal (START). Low to high pulse at START will start conversion of analog input into digital.

User can check whether conversion is complete or not through EOC [End of conversion].

EOC → 0 → when conversion completed

EOC → 1 → when conversion is going on

User can continuously check EOC is 0 or not. If 0 that means conversion is completed (Analog Data is converted to Digital)

Digital o/p is stored in the internal Register of ADC IC.

To place this Digital o/p on Digital bus user has to send OE (Output Enable signal)

Low to high pulse should be given to OE signal to place Digital o/p on Digital / Data bus.

ADC has 8 bit Digital bus. ($D_0 - D_7$)
o/p will be available on $D_0 - D_7$.

operation of IC is carried out using CLOCK
clock can be generated using external circuit
OE 8051 clock can be connected to
ADC 0808/0809 CLOCK pin.

$V_{CC} \rightarrow +5V$ supply
 $GND \rightarrow GND$

$V_{ref}(+)$ \rightarrow +ve voltage.

$V_{ref}(-) \rightarrow GND$

Input / output Relation :

8 bit ADC

$$\text{Steps} = 2^8 = 256$$

Digital o/p

0000	0000
0000	0001
⋮	⋮
⋮	⋮
1111	1111

Total 256 steps
for Digital o/p.

Step size : how much analog input should change to change Digital o/p by one step.

$$\text{Step size} = \frac{V_{ref}}{2^8} \quad \text{consider } V_{ref} = 2.56 \Rightarrow \frac{2.56}{256} = 10 \text{ mV}$$

If i/p analog voltage change by 10 mV, Digital o/p will change by 1 step.

$$\text{O/P in decimal} = V_{in} \times \frac{256}{V_{ref}}$$

Assume
Analog i/p voltage = 1 V

$$V_{ref} = 2.56 \text{ V}$$

$$\text{O/P} = 1 \times \frac{256}{2.56} = (100)_{10}$$

$$= (0110 \quad 0100)_2 = 64 \text{ H}$$

Interfacing Diagram of ADC 0808/0809 to 8051 UC

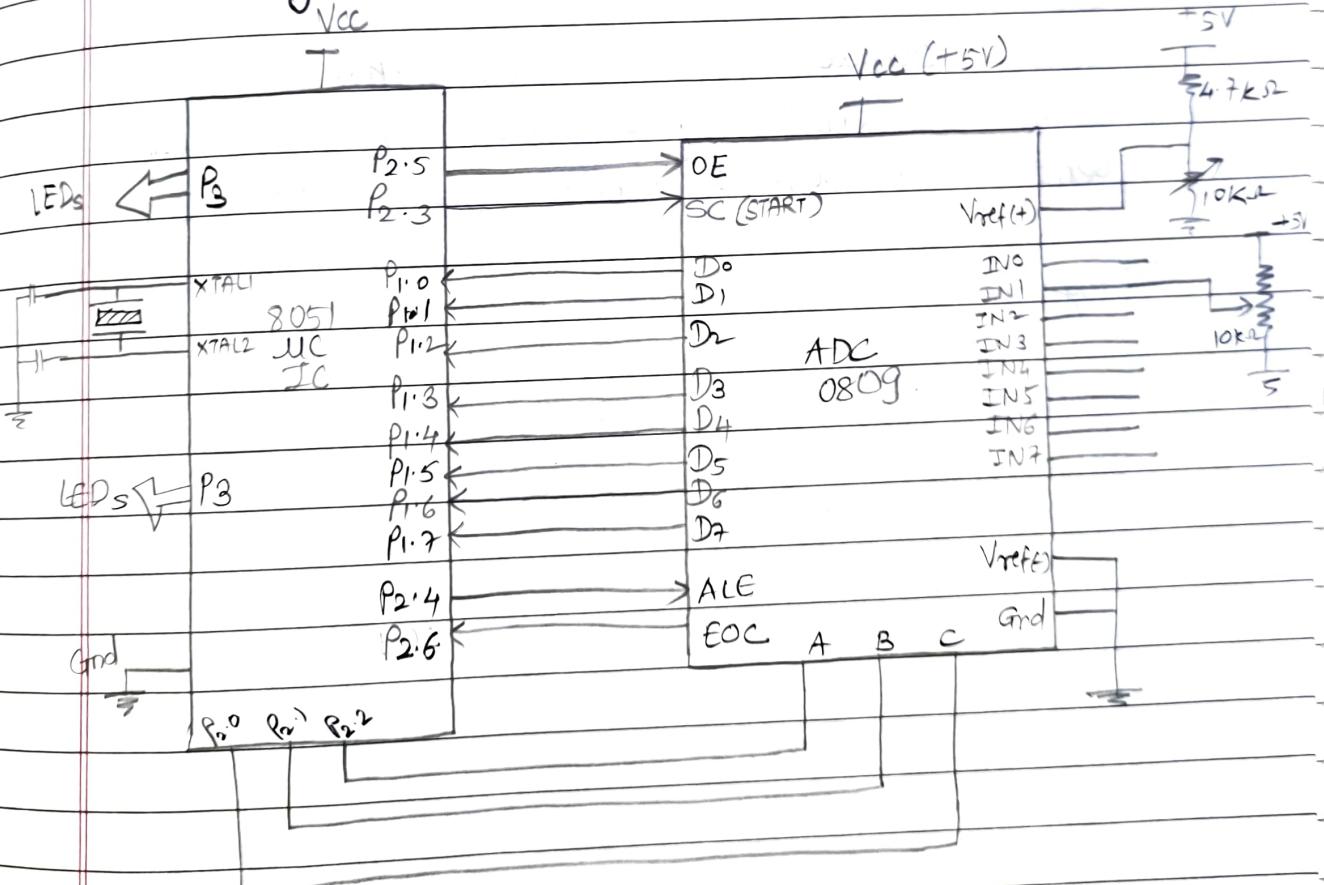


fig: 8051 Connections to ADC 0808/0809.

Algorithm :

- 1) Send logic 1 at Port 1 all terminals and P2.5 pin
(This pins are used as i/p pins to 8051)
- 2) Connect analog i/p voltage at IN1
- 3) Send address of channel on address line (A,B,C)
i.e 001 (channel 1)
- 4) Send ALE to latch address (L-H)
- 5) send start of conversion signal (L-H)
- 6) wait for EOC . IF EOC is 0 then go to next step .
- 7) Send output Enable (OE) signal (L-H)
- 8) Read converted Digital data from P1 and send it on port 3. where LEDs are connected.

Program :

```

⑥ #include <reg51.h>
sbit ALE P2^4;
sbit OE P2^5;
sbit SC P2^3;
sbit EOC P2^6;
sbit A = P2^2
sbit B = P2^1
sbit C = P2^0

```

Sfr mybyte = B ; . . . ;
 Sfr senddata = P3 ; // LED's are connected

```

Void dataconversion (unsigned char);
Void display ( unsigned char );
Void delay ( );

```

① void main ()

{

unsigned char Value ;

A = 0 ;

B = 0 ;

C = 0 ;

ALE = 0 ;

OE = 0 ;

EOC = 1

mybyte = 0xFF

} // D/P pin

// i/p pin

// i/p port.

while (1) :

{

A = 1 ; // select analog i/p channel.

B = 0 ;

INT = 001

C = 0 ;

// High pulse on ALE

delay ();

SC = 1 ;

// start conversion

delay ();

ALE = 0 ;

// Low pulse on ALE

SC = 0 ;

// Low pulse on SC

while (EOC == 1);

// wait for data conversion

while (EOC == 0);

OE = 1 ;

Value = mybyte ;

senddata = Value ;

// H-L on OE

OE = 0 ;

② void delay ()

{

int j ;

for (j=0; j<1000; j++)

{

}

}

→ **DAC**

NC	1	16	compensation
GND	2	15	V_{ref}^-
VEE	3	14	V_{ref}^+
IO	4	DAC 13	VCC
D ₁	5	0808 12	D ₈
D ₂	6	11	D ₇
D ₃	7	10	D ₆
D ₄	8	9	D ₅

fig: pin diagram of DAC 0808

D₀ - D₇ : Digital input

D₀ D₁ D₂ D₃ D₄ D₅ D₆ D₇

MSB

LSB

D₀ - D₇ are connected to Microcontroller

Analog o/p will be available on pin 4 of DAC 0808

Analog o/p is in the form of Current.

Externally we need to connect current to voltage converter which converts output current in voltage
We obtain voltage analog signal

Pin 2 Ground

Pin 13 Vcc (+ve supply of 5V)

Pin 3 VEE (-ve supply, Generally connected to Ground)

Pin 14 V_{ref} + (positive reference voltage)
+5 or +10 V can be applied

The o/p cln depends on value of V_{ref} +

Pin 15 V_{ref} - (-negative reference voltage)
Generally connected to Ground

Pin 16 Compensation

Capacitor can be connected at this pin to reduce noise

Pin 1 Not connected

Input Output Relation:

$$I_o = I_{ref} \left[\frac{D_0}{2} + \frac{D_1}{4} + \frac{D_2}{8} + \frac{D_3}{16} + \frac{D_4}{32} + \frac{D_5}{64} + \dots + \frac{D_n}{2^n} \right]$$

$$V_o = I_o \times R \rightarrow 2.5 \text{ k}\Omega$$

Date 12/8
Page _____

Interfacing DAC 0808 to 8051

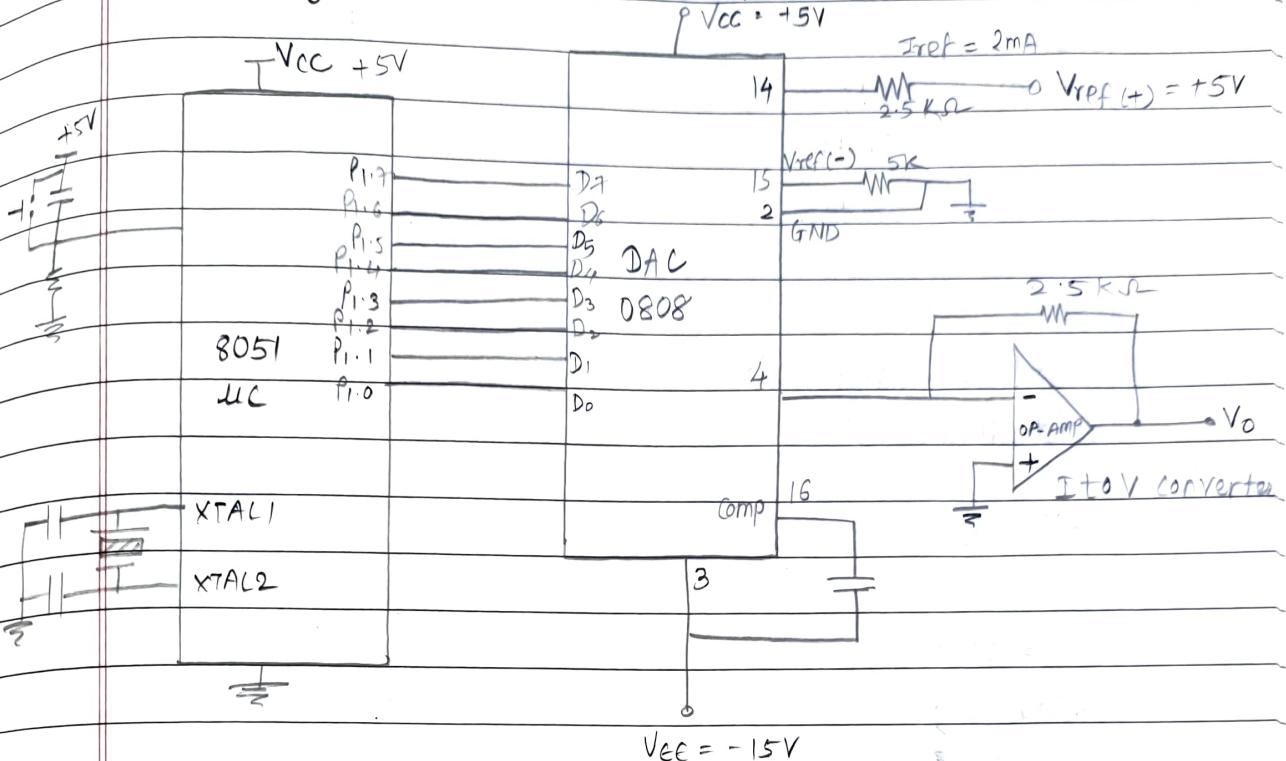


fig: Interfacing Diagram of 0808 DAC to 8051 Microcontroller

Program to Generate square wave:

```
#include <reg51.h>
void delay();
Void main()
{
```

```
while (1)
```

```
{
```


```
P1 = 0xFF;
```

```
delay();
```

```
P1 = 0x00;
```

```
delay();
```

```
{
```

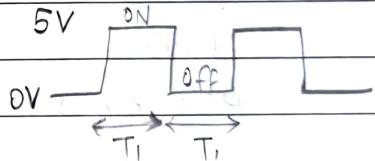

```
Void delay ()
{int i;
for (i=0 ; i<1000; i++)
{}}
```

if i/p 00H \Rightarrow I_o = 0A

$$V_o = 0 \times 2.5\text{k} = 0\text{V}$$

if i/p ff \Rightarrow I_o = $2\text{mA} \left[\frac{1}{2} + \frac{1}{4} + \frac{1}{8} + \frac{1}{16} + \frac{1}{32} + \frac{1}{64} + \frac{1}{128} + \frac{1}{256} \right]$

$$I_o = 2\text{mA}$$


$$V_o = 2.5\text{k} \times 2\text{mA} = 5\text{V}$$

Program to generate staircase waveform:
 logic:

for $0V = 00H$

for $2.5V = 7FH$

for $5V = FFH$.

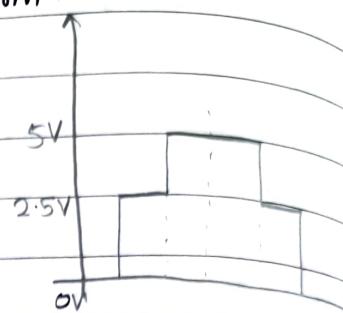

#include <reg51.h>
 Void delay();

Void main ()
 {

P1 = 0x00;

delay();

P1 = 0xFF;

delay();

P1 = 0x00;

delay();

delay();

P1 = 0xFF;

delay();

}

Void delay ()
 {

int i;

for (i=0; i<1000; i++)

{

}

L Relay :

Relay is an electrically controllable switch.

Microcontroller use relays to control a heavy electrical load.

Relay allows isolation between high power and low power sections of a system having different voltage sources.

Operating voltage : 5V, 6V, 12V, 24V


Basic Types of Relay :

Electromechanical Relays :


- They have coils, spring and contact
- Switching is slow
- Generates noise.

Solid State Relays :

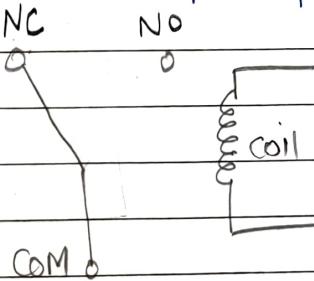- Uses semiconductor devices for switching
- No movable parts and higher life cycle.
- faster switching time
- use of optocouplers provide electrical isolation & control



coil Not Energised
Relay off

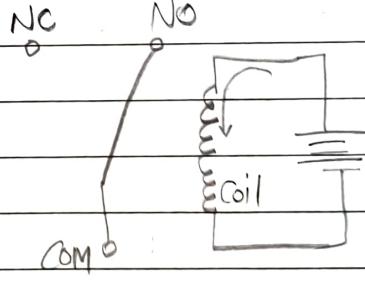

coil is Energised
Relay on

coil : Energise when given voltage

COM : Common Terminal

NO : Normally open Terminal

NC : Normally close Terminal

Relay off \rightarrow COM connected to NC

Relay on \rightarrow COM connected to NO.

why driver circuit is needed for interfacing Relay?


A Microcontroller is not able to supply current required for the proper working of relay.

The back emf produced by relay coil can damage port pins.

freewheeling diode is used to suppress back emf.

Driver circuitry can be implemented using power transistor & Diode, ICs

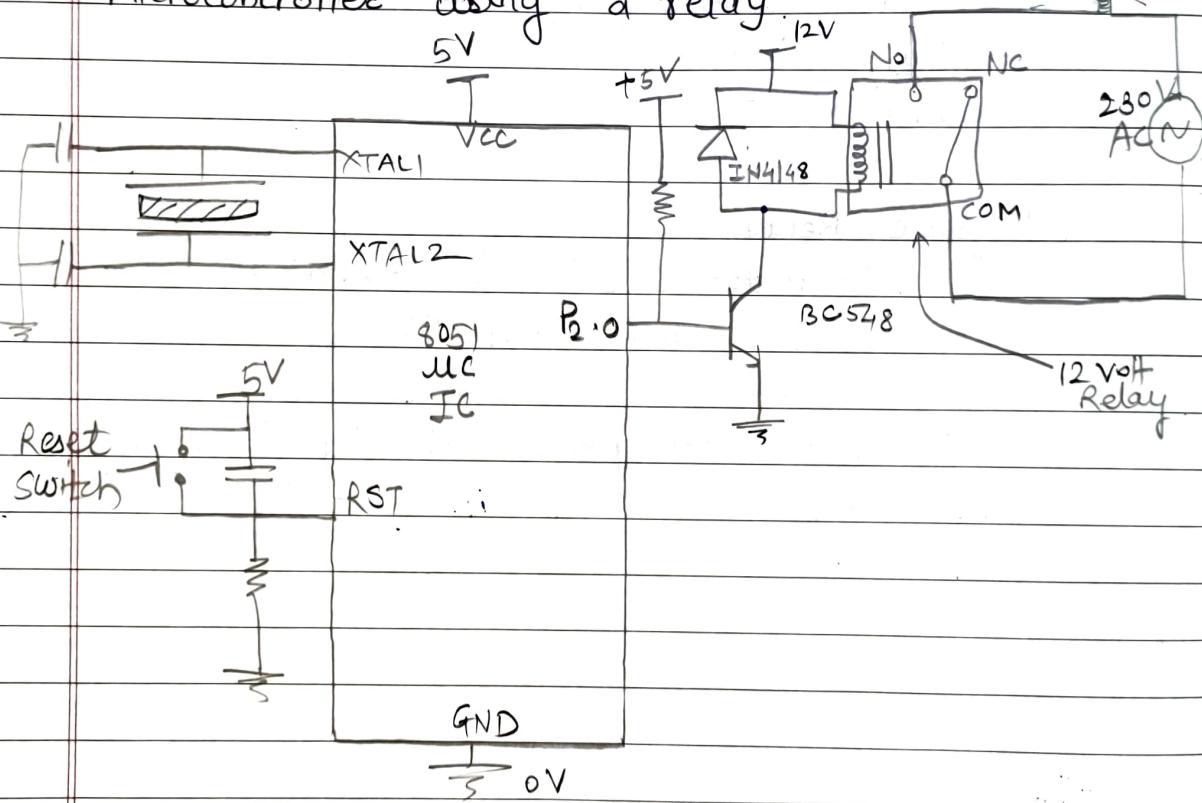Interfacing a bulb working on 230V AC supply to Microcontroller using a relay



When $P2.0 = 1 \rightarrow 1$ on the Base of (npn) Transistor make Transistor ON, this will connect coil terminal to Ground \rightarrow Relay gets supply and coil gets energised \rightarrow As a result COM terminal breaks from NC and gets attracted to NO terminal & bulb gets power (ON)

when $P2 \cdot 0 = 0$, transistor off \rightarrow disconnect coil from Ground so coil gets deenergised and com terminal which is connected to NO terminal will get attracted back to NC \rightarrow this disconnect the bulb from one end of power supply hence bulb gets turned OFF.

c program:

```
#include <reg51.h>
void delay()
sbit relay = P2^0;


Void main()
{
    relay = 0; // P2.0 as output port.
    while(1)
    {
        relay = 1; // Relay ON  $\rightarrow$  Bulb ON
        delay();
        relay = 0; // Relay off  $\rightarrow$  Bulb off
        delay();
    }
}

void delay()
{
    int i,j;
    for (i=0; i<10; i++)
    {
        for (j=0 ; j < 1000; j++)
    }
}
```

Relay interfacing with 8051 using ULN2003 Driver (Refer PPT for Diagram)

VLN 2003 - Seven relays can be interfaced.

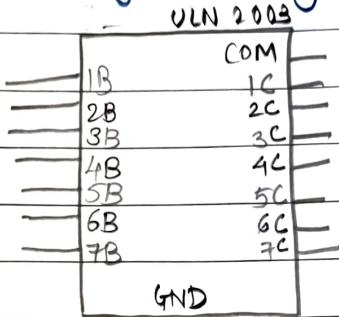
ULN 2803 - Eight relays can be interfaced.



L

Buzzer:

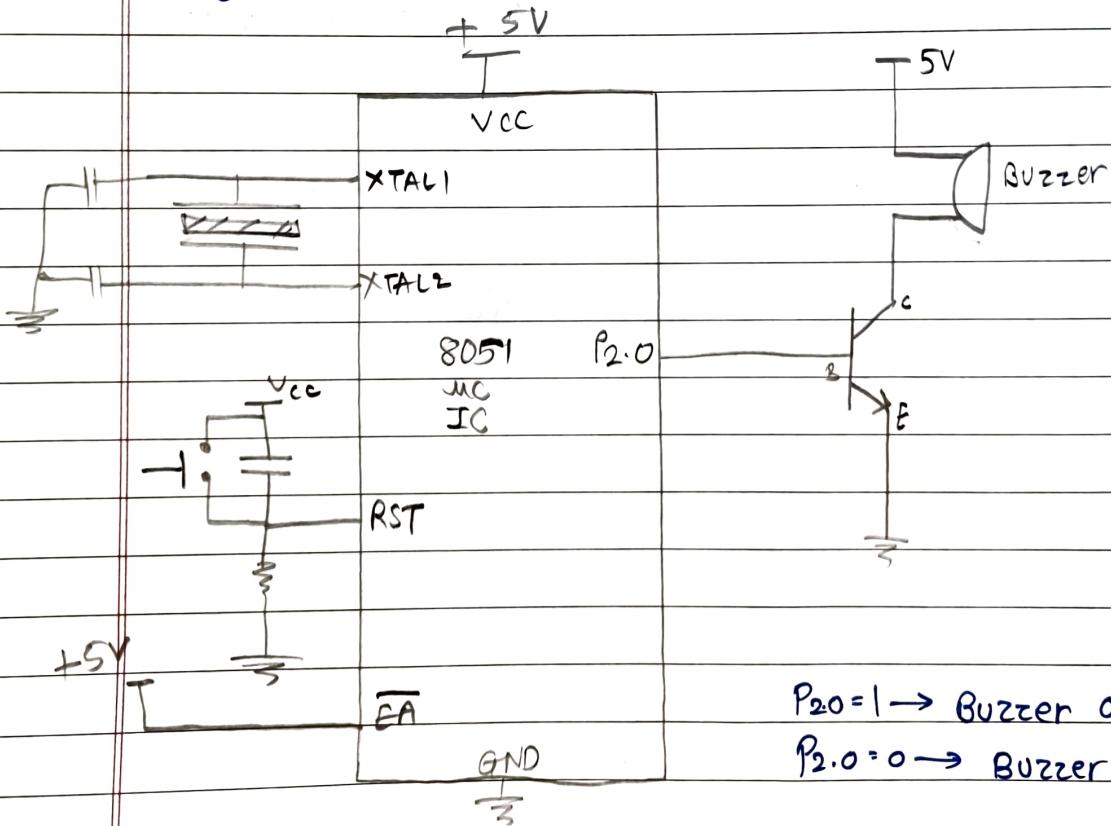A Buzzer is an audio signalling Device which may be mechanical, electromechanical or piezoelectric.



```
#include <reg51.h>
void delay();
Sbit pin_buzzer = P2^0;


Void main()
{while (1)
{
    pin_buzzer=0; // Buzzer off
    delay();
    pin_buzzer = 1; // Buzzer ON .
    delay();
}
}

Void delay()
{
int i,j;
for (i=0 ; i<20;i++)
{
    for (j=0 ; j<1000;j++)
}
}
```



Opto Isolator

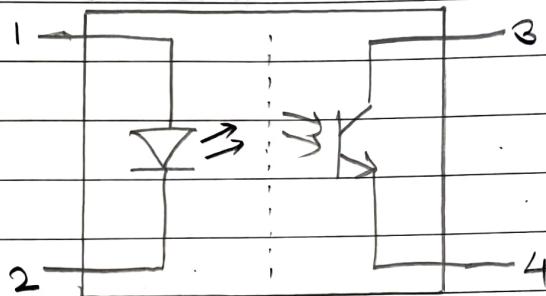In electronics, an opto isolator are called an optocoupler, photocoupler or optical isolator is a component that transfers electrical signal between two isolated circuits by using light. Opto Isolator prevents high voltages from affecting the system receiving the signal. Commercially available opto isolators withstand i/p to o/p voltages upto 10 KV & voltage transients with speeds upto 10 KV/us.



A common type of opto isolator consist of an LED and photo transistor. Other type of source - sensor combination include LED - photodiode, LED - LASCR, lamp - photistor.

Usually opto isolator transfer digital signals.

Rating of opto isolator depends on output voltage drive capacity of opto isolator. (30V, 70V & 80V are commonly used O/p voltage Ratings).

4N25, 4N26, ILD74, PC817 are mostly used opto isolator.

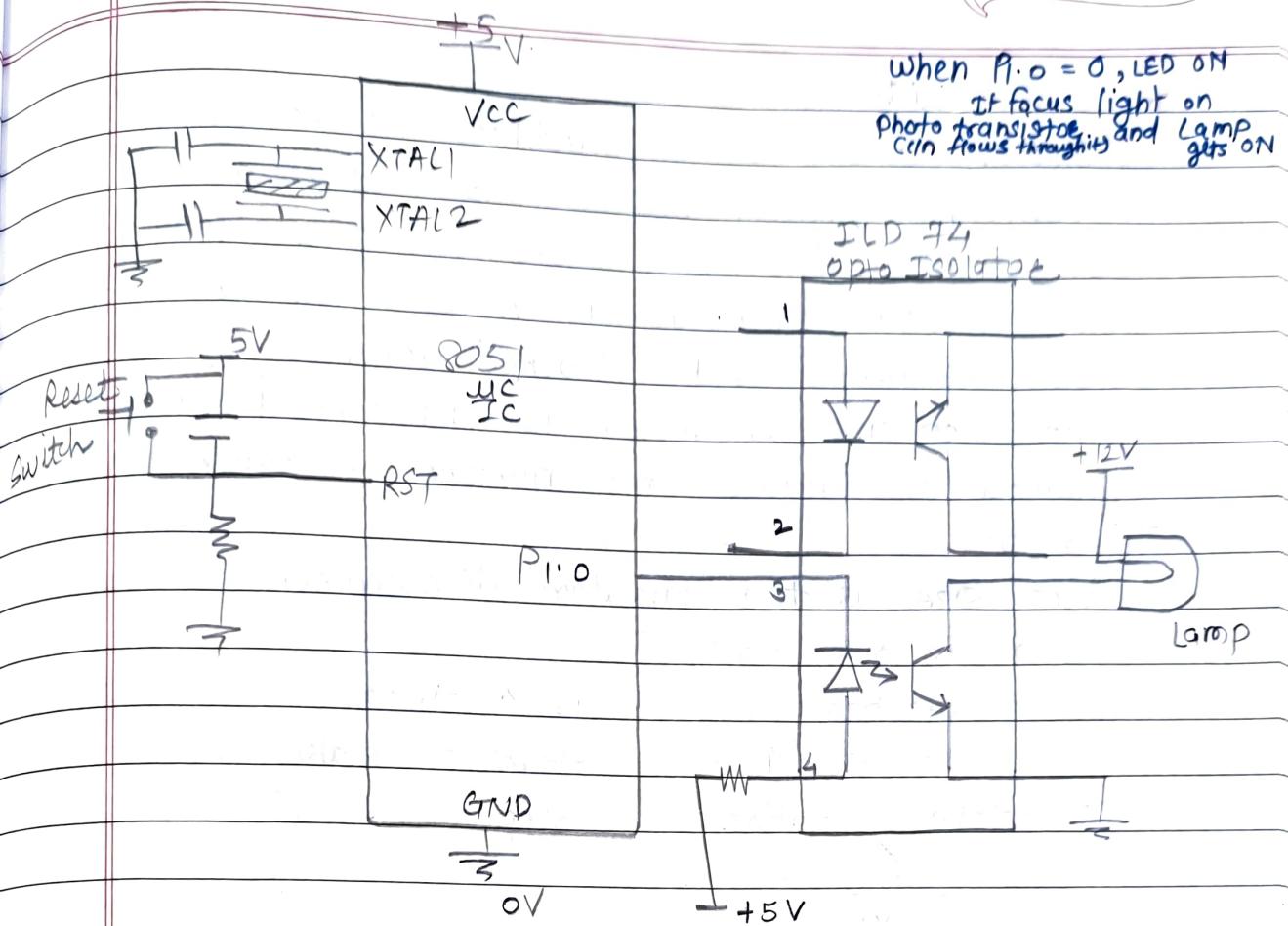


fig: Interfacing Diagram of Opto Isolator with 8051

```
#include <reg51.h>
```

```
void delay();
```

```
sbit opt_iso = P1^0;
```

```
void main()
```

```
{
```

```
while(1)
```

```
{
```

```
opt_iso = 0;
```

```
// Lamp ON
```

```
delay();
```

```
opt_iso = 1;
```

```
// Lamp OFF
```

```
delay();
```

```
}
```

```
void delay()
```

```
{
```

```
int i;
```

```
for (i=0; i<1000; i++)
```

```
{
```

```
}
```

```
}
```

L ↳ Stepper Motor:


Stepper Motor is a brushless Motor which converts electrical pulses into Mechanical rotation. It rotates in steps according to the input pulses. A stepper motor usually have a number of field coil (phases) and a toothed rotor.

The step size of motor is determined by the number of phases and number of teeth on the rotor.

Step size is the angular displacement of the rotor in one step.

If a stepper motor has 4 phases and 50 teeth, it takes $50 \times 4 = 200$ steps to make one complete rotation. so step angle will be


$$\frac{360}{200} = 1.8^\circ.$$

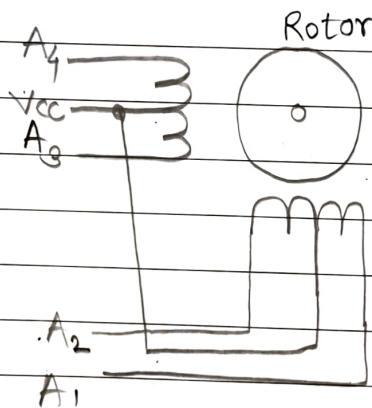

- A1 = phase 1
- A2 = phase 2
- A3 = phase 3
- A4 = phase 4.

To Rotate this motor we have to give excitation to each phase in proper order.

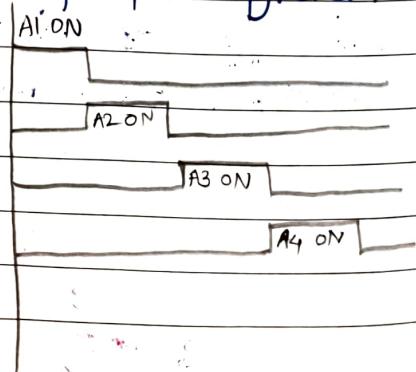The stepper motor is rotated by switching individual phase ON for a given time one by one



Stepper Motor step angles .

Step angle	steps per Revolution
0.72	500
1.8	200
2.0	180
2.5	144
5.0	72
7.5	48
15	24

Generally this
step angle
motor is
used

$$\text{Steps per second} = \frac{\text{rpm} \times \text{steps per Revolution}}{60}$$

Modes to Drive Stepper Motor :

full step Mode : Two electromagnets are energised at a single time

Torque which is generated will be greater.
Power Consumption is higher in it.

This type of mode is chosen when the torque is more important than power Consumption.

Half Step Mode : one electromagnet is energized in this mode.

It has low torque but the angular resolution is doubled

This type of drive is chosen when we want to increase the angular resolution of the motor.

full step Mode

Step	A	B	C	D
1	1	1	0	0
2	0	1	1	0
3	0	0	1	1
4	1	0	0	1


Anticlockwise ↑
↓ Clockwise

Half step Mode

Step	A	B	C	D
1	1	0	0	0
2	1	1	0	0
3	0	1	0	0
4	0	1	1	0
5	0	0	1	0
6	0	0	1	1
7	0	0	0	1
8	1	0	0	1

Anticlockwise ↑
↓ Clockwise

Fig: Interfacing of 8051 with stepper Motor

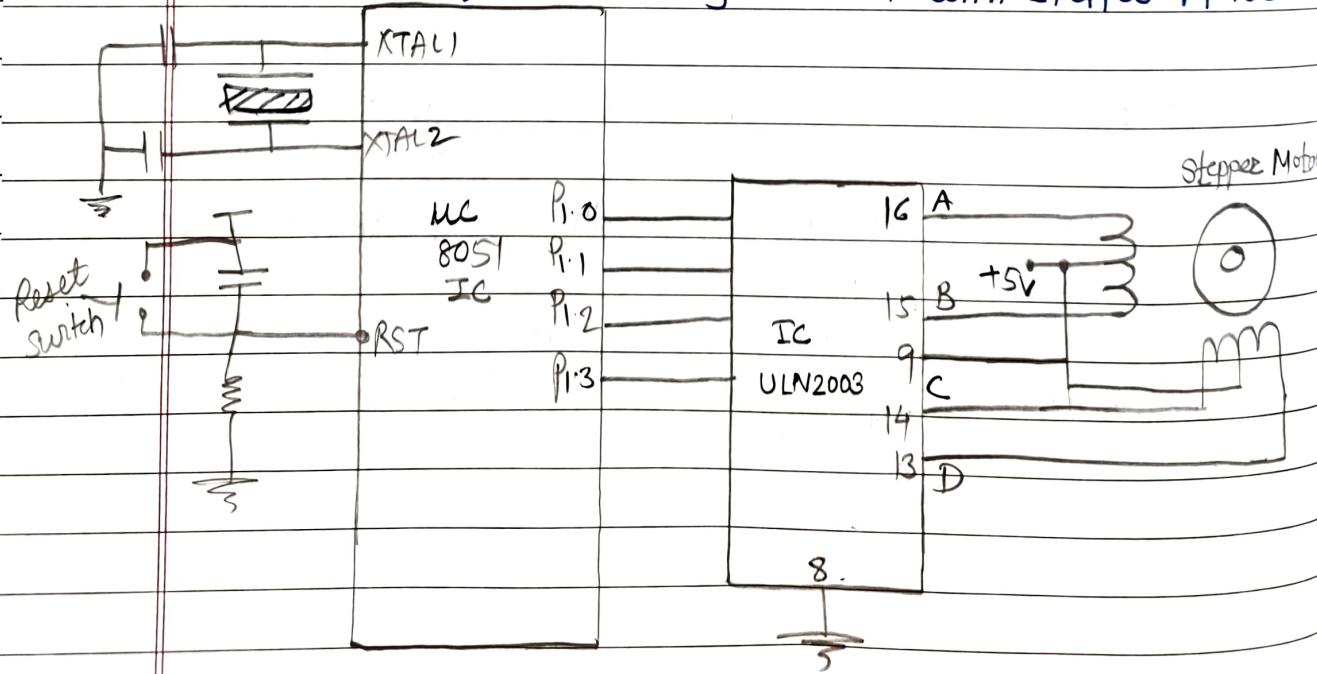

ULN2003 → Driver IC

Used for Driving individual phases of Motor

It is Darlington transistor array IC

It is used for driving high current loads such as relays, Motor

It has 8 individual channels, each channel with 1Ampere capacity.

	P1	P1.7	P1.6	P1.5	P1.4	P1.3	D	C	B	A
03H	X	X	X	X	X	0	0	0	1	1
06H	X	X	X	X	X	0	1	1	0	0
0CH	X	X	X	X	X	1	1	0	0	0
09H	X	X	X	X	X	1	0	0	0	1

clockwise

C program to rotate stepper motor clockwise in full step mode

```
#include <reg51.h>
```

```
Void delay();
```

```
Void main()
```

```
{ P1 = 0X00;
```

//P1 as output

```
while(1)
```

```
{
```

```
    P1 = 0X03;
```

```
    delay();
```

```
    P1 = 0X06;
```

```
    delay();
```

```
    P1 = 0X0C;
```

```
    delay();
```

```
    P1 = 0X09;
```

```
    delay();
```

```
}
```

```
void delay()
```

```
{ int i,j;
```

```
for (i=0;i<100;i++)
```

```
{
```

```
for (j=0;j<1275;j++)
```

```
{
```

```
}
```

```
}
```

C program to rotate Stepper Motor in clockwise direction with Half stepping Mode.

	D	C	B	A	P1.Val _{4..0}	
P1.7	X	X	X	X	0	01H
P1.6	X	X	X	X	0	03H
P1.5	X	X	X	X	0	02H
P1.4	X	X	X	X	1	06H
P1.3	X	X	X	X	1	04H
P1.2	X	X	X	X	1	0CH
P1.1	X	X	X	X	0	08H
P1.0	X	X	X	X	0	09H

```
#include <reg51.h>
```

```
void delay();
```

```
void main()
```

```
{ while(1) {
```

```
    P1 = 0X01;
```

```
    delay();
```

```
    P1 = 0X03;
```

```
    delay();
```

```
    P1 = 0X02;
```

```
    delay();
```

```
    P1 = 0X06;
```

```
    delay();
```

```
    P1 = 0X04;
```

```
    delay();
```

```
    P1 = 0X0C;
```

```
    delay();
```

```
    P1 = 0X08;
```

```
    delay();
```

```
    P1 = 0X09;
```

```
} delay();
```

```
void delay()
```

```
{
```

```
int i,j;
```

```
for (i=0 ; i<100 ; i++)
```

```
{
```

```
for (j=0 ; j<1275 ; j++)
```

```
{
```

```
{
```

```
}
```

```
{
```

► Keys :

A Keyboard is arranged as an array of switches


- mechanical
- Membrane
- Capacitors
- Hall effect in construction.

Mechanical switches are most popular for keyboards.

- mechanical switches have a problem called contact bounce. closing a mechanical switch generates a series of pulse because the switch contacts do not come to rest immediately.

- In addition a human cannot type more than 50 keys in a second. Reading a keyboard more than 50 times a second will read the same key stroke too many times.

↳

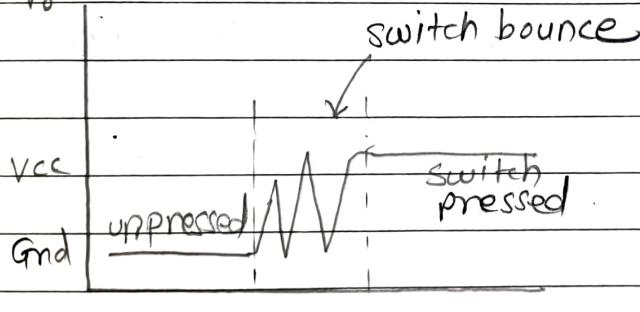

When we press a pushbutton or toggle switch two metal parts come into contact to short the supply.

But they don't connect instantly, the metal parts connect & disconnect several times before the actual connection is made.

The same thing happens while releasing the button. This results in false or multiple triggering like the button is pressed multiple times.

It's like falling a bouncing ball from a height & it keeps bouncing on surface until it comes to rest.

switch bouncing :



switch bouncing is the non ideal behavior of any switch which generates multiple transitions of single i/p.

switch bouncing cause problems while we are dealing with logic or digital circuits.
Hence to remove the bouncing from the circuit debouncing circuit is used.


Two types of debouncing :

- ① Software Debouncing → add delays, interrupt.
- ② Hardware Debouncing.

Interfacing Simple keys to 8051

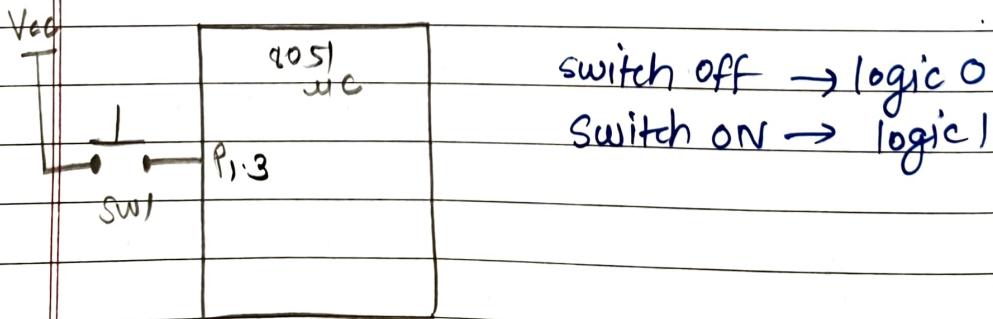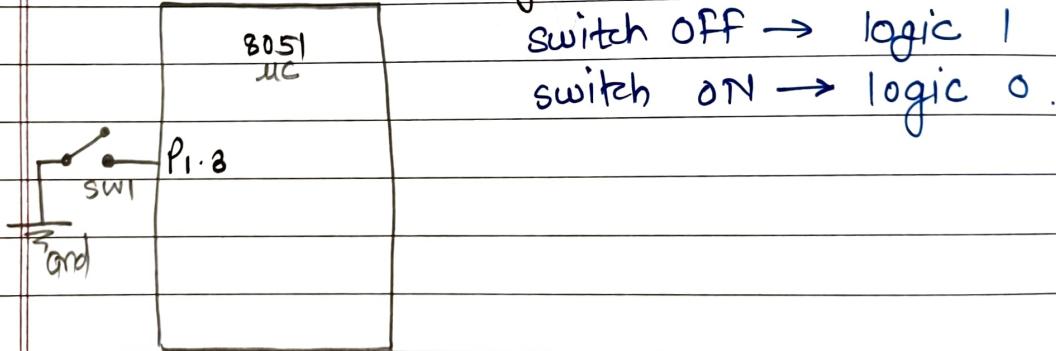

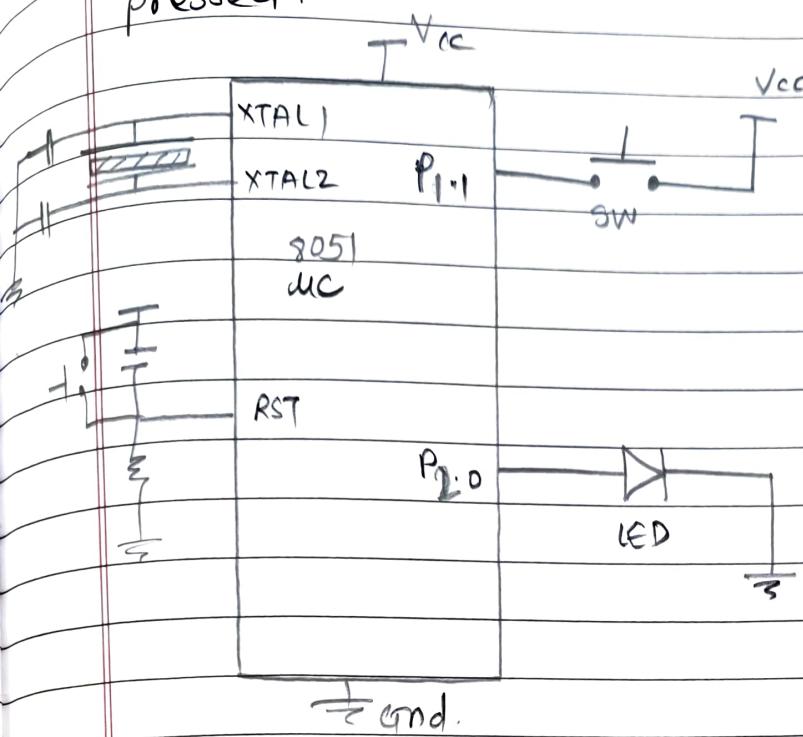8051 C program to blink LED connected on P2.0 when switch connected on P1.1 is pressed.



```
#include <reg51.h>
sbit LED = P2^0;
sbit switch = P1^1;
```

```
void main()
{
    P0 = 0xFF; // P0 as i/p port.
    while(1)
    {
        if (switch == 1)
            LED = 1;
        else
            LED = 0;
    }
}
```